



T.J.S ENGINEERING COLLEGE

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai.

Accredited by NAAC / ISO 9001:2015 Certified Institution

TJS Nagar, Peruvoyal, Near Kavaraipettai, Gummidipoondi Taluk, Thiruvallur District -601206




2.2.1. QIM	The institution assesses the learning levels of the students and organizes special Programmes for advanced learners and slow learners
-----------------------	--

Assignments

LIC Assignment - 1

Ideal Differentiator :-

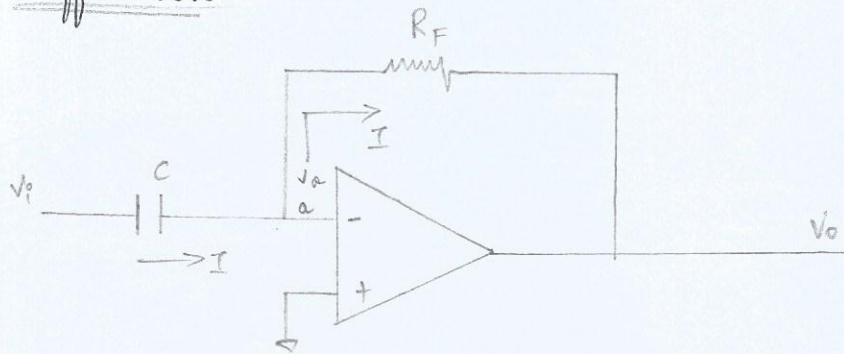

The o/p voltage (V_o) produces the Differentiation of i/p voltage V_i .

Nodal equation at 'a',

$$C_F \frac{d(V_i - V_a)}{dt} + \frac{V_o - V_a}{R_F} = 0$$

Assume $V_a = 0$,

$$C \frac{dV_i}{dt} + \frac{V_o}{R_F} = 0$$

$$\frac{V_o}{R_F} = -C \frac{dV_i}{dt}$$

$$V_o = -C R_F \frac{dV_i}{dt}$$

PRINCIPAL

T.J.S. ENGINEERING COLLEGE


Peruvoyal, Kavaraipeetai,

Gummidipoondi Taluk,

Thiruvallur Dist - 601 206.



Ideal Integrator:-

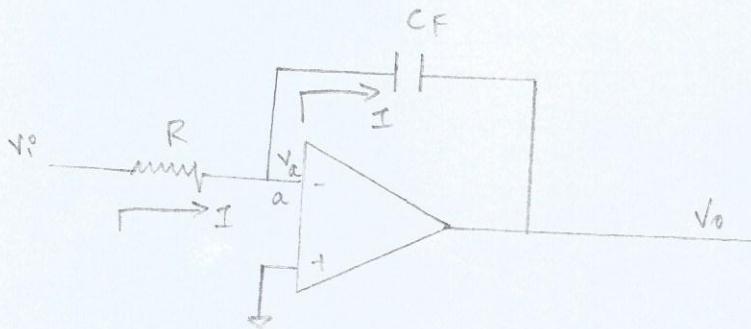

The O/P Voltage (v_o) produces the integration of voltage (v_i).

Nodal equation at 'a'

$$\frac{v_i - v_a}{R} + C_F \frac{d(v_o - v_a)}{dt} = 0$$

Assume $v_a = 0$,


$$\frac{v_i}{R} + C_F \frac{dv_o}{dt} = 0$$

$$C_F \frac{dv_o}{dt} = - \frac{v_i}{R}$$

Taking integral on both side,


$$\int dv_o = - \int \frac{v_i dt}{RC_F}$$

$$v_o = - \frac{1}{RC_F} \int v_i dt$$

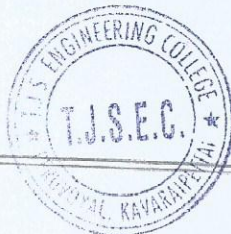

S. Kumar
PRINCIPAL
T.J.S. ENGINEERING COLLEGE
Peruvoyal, Kavaratp...
Gummidipoondi Taluk
Thiruvallur Dist - 601 206.

Practical Differentiator:-

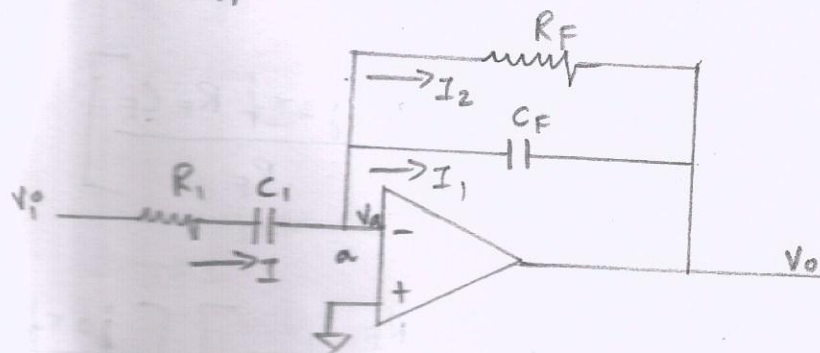

Nodal equation at 'a'

$$I = I_1 + I_2$$

$$\frac{V_i - V_a}{R_1 + 1/j\omega C_1} = C_F \frac{d(V_a - V_o)}{dt} + \frac{V_a - V_o}{R_F}$$

assume $V_a = 0$,

$$\frac{V_i}{R_1 + 1/j\omega C_1} = -C_F \frac{dV_o}{dt} - \frac{V_o}{R_F}$$

Taking Laplace transform,

$$\frac{V_i(s)}{j\omega R_1 C_1 + 1} = -C_F s \cdot V_o(s) - \frac{V_o(s)}{R_F}$$

$$\frac{V_i(s)}{j\omega R_1 C_1 + 1} = -V_o(s) \left[\frac{1}{R_F} + s C_F \right]$$

$$\frac{V_i(s)}{j\omega R_1 C_1 + 1} = -V_o(s) \left[\frac{1 + s C_F R_F}{R_F} \right]$$




[Signature]

PRINCIPAL

T.J.S. ENGINEERING COLLEGE
Peruvoyal, Kavaraipeitai,
Gummidipondi Taluk.

Practical Integrator:-

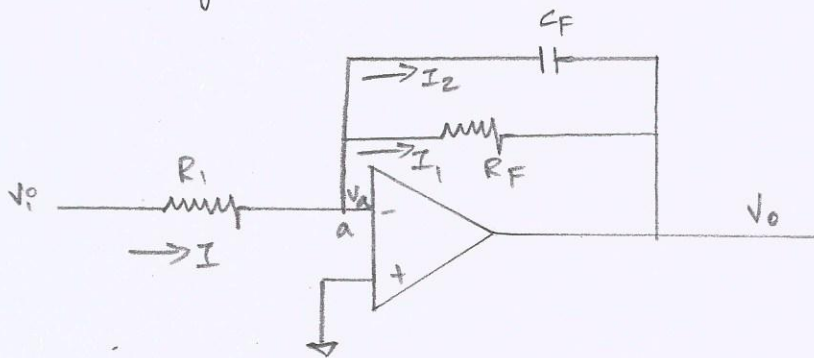

Nodal equation at 'a',

$$I = I_1 + I_2$$

$$\frac{V_i - V_a}{R_1} = \frac{V_a - V_o}{R_F} + C_F \frac{d(V_a - V_o)}{dt}$$

assume $V_a = 0$,

$$\frac{V_i}{R_1} = \frac{-V_o}{R_F} - C_F \frac{dV_o}{dt}$$

Taking laplace transform,

$$\frac{V_i(s)}{R_1} = \frac{-V_o(s)}{R_F} - C_F s \cdot V_o(s)$$

$$\frac{V_o(s)}{V_i(s)} = - \left[\frac{R_F}{1 + s C_F R_F} \right] \frac{1}{R_1}$$

Put $s = j\omega$, $\omega = 2\pi f$

$$A = \frac{V_o(s)}{V_i(s)} = - \left[\frac{R_F/R_1}{1 + j2\pi f C_F R_F} \right]$$

$$= - \left[\frac{R_F/R_1}{1 + j \frac{1}{F_H}} \right]$$

$$|A| = \left[\frac{R_F/R_1}{1 + \frac{1}{F_H^2}} \right]$$



PRINCIPAL

T.J.S. ENGINEERING COLLEGE
Peruvoyal, Kavaraipeetai,
Gummidipoondi Taluk,
Thiruvallur Dist - 601 206.